

Assignment 1 (EC-262)

Question 1. Design a Full subtractor using a 2 to 4 decoder

Question 2. Implement $f(A,B,C)=\sum m(0,1,3,5,6,7)$ using 4x1 multiplexer with

- a. AB as select line
- b. AC as select line
- c. BC as select line

Question 3. Convert the following :

- a. Octal to Binary : 1204, 743
- b. Binary to Gray : 11011
- c. Gray to Binary : 11011
- d. Binary to Excess 3 code : 1001 0111
- e. Perform the BCD addition of 365 & 784
- f. Perform the below operation in 2's complement form
 - 1) $(-14)-(36)$
 - 2) $-14-(-36)$

Question 4. Design a signed bit comparator which compares two sequence of 3 bits.

Question 5. Design a BCD to 7 Segment Decoder. Write down the Boolean expression of all the segments along with their individual truth table.