

RITIK SINGH

# DIGITAL ELECTRONICS

2K19/CO/319

## ASSIGNMENT-2

Q1	Clock Pulse	Register Contents	Next Operation
	0	01001100	Shift left
	1	10011000	Shift right
	2	01001100	Shift right
	3	00100110	Shift right
	4	00010011	Shift left
	5	00100110	Shift left
	6	01001100	Shift right
	7	00100110	Shift left
	8	01001100	Shift right
	9	00100110	Shift left
	10	01001100	Shift left
	11	10011000	

Q2 Sequence: 00, 10, 01, 11, 00

i) Using J-K FF

Since all numbers are 2 bit no therefore we need 2 JK Flip Flop.

Present	State	Next state	FF				
A	B	A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	1	0	1	X	0	X
1	0	0	1	X	1	1	X
0	1	1	1	1	X	X	0
1	1	0	0	X	1	X	1

$J_A \rightarrow$

A \ B	$\bar{B}$	B
$\bar{A}$	1 <sub>0</sub>	1 <sub>1</sub>
A	X <sub>2</sub>	X <sub>3</sub>

$\Rightarrow J_A = 1$

$K_A \rightarrow$

A \ B	$\bar{B}$	B
$\bar{A}$	X <sub>0</sub>	X <sub>1</sub>
A	1 <sub>2</sub>	1 <sub>3</sub>

$\Rightarrow K_A = 1$

$J_B$


A \ B	$\bar{B}$	B
$\bar{A}$	0 <sub>0</sub>	X <sub>1</sub>
A	1 <sub>2</sub>	X <sub>3</sub>

$\Rightarrow J_B = A$

$K_B$

A \ B	$\bar{B}$	B
$\bar{A}$	X <sub>0</sub>	0 <sub>1</sub>
A	X <sub>2</sub>	1 <sub>3</sub>

$\Rightarrow K_B = A$

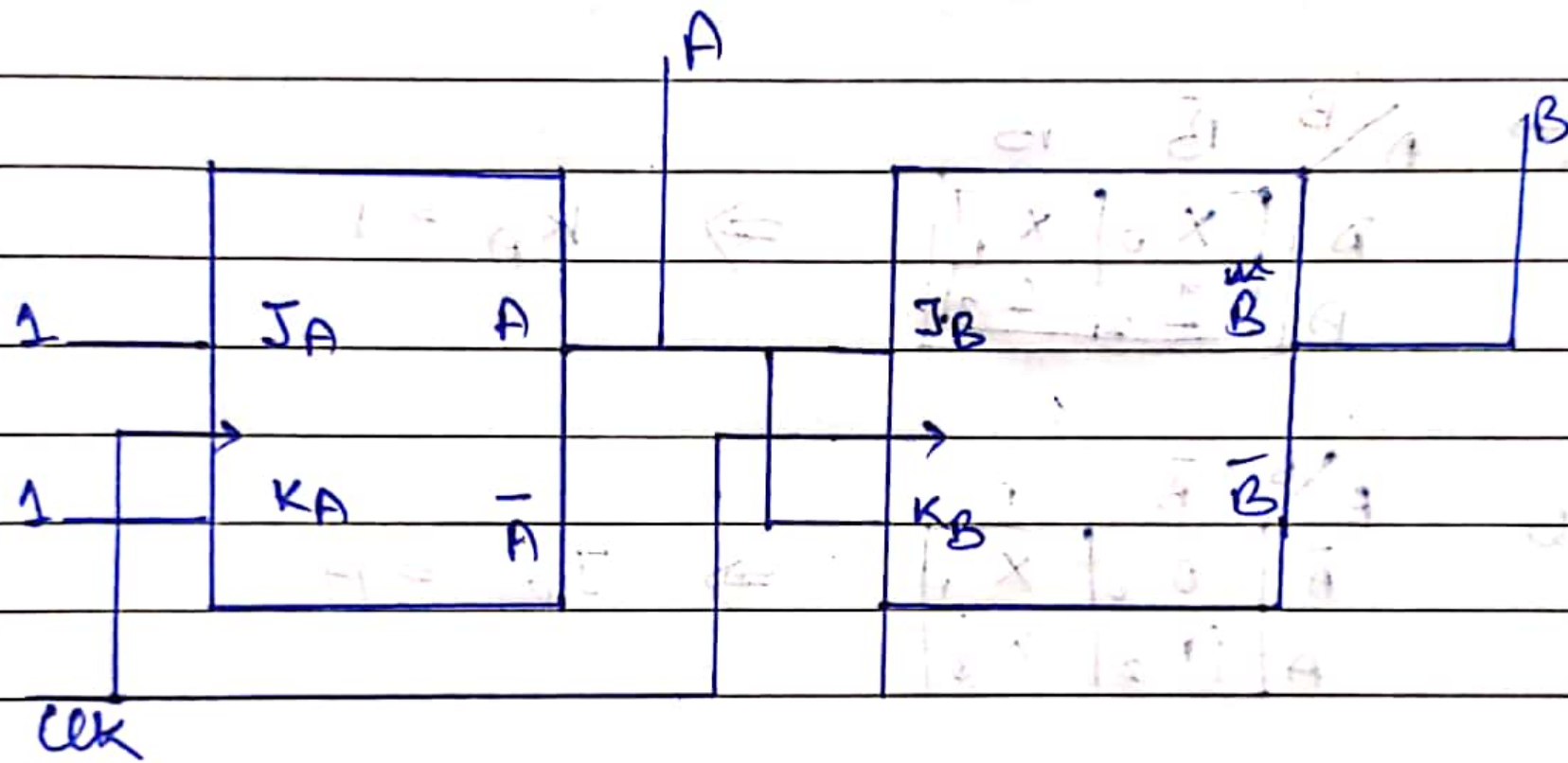

A is MSB and B is LSB



ii) Using DFF

Present State		Next State		FF	
A	B	A	B	D <sub>A</sub>	D <sub>B</sub>
0	0	1	0	1	0
2	1	0	1	0	1
1	0	1	1	1	1
3	1	0	0	0	0

For D<sub>A</sub>:

A \ B	$\bar{B}$	B
$\bar{A}$	1 <sub>0</sub>	1
A	0 <sub>2</sub>	0 <sub>3</sub>


$$\Rightarrow D_A \Rightarrow \bar{A}$$

For D<sub>B</sub>:

A \ B	$\bar{B}$	B
$\bar{A}$	0 <sub>0</sub>	1 <sub>1</sub>
A	1 <sub>2</sub>	0 <sub>3</sub>


$$= \bar{A}B + A\bar{B}$$

$$= A \oplus B$$

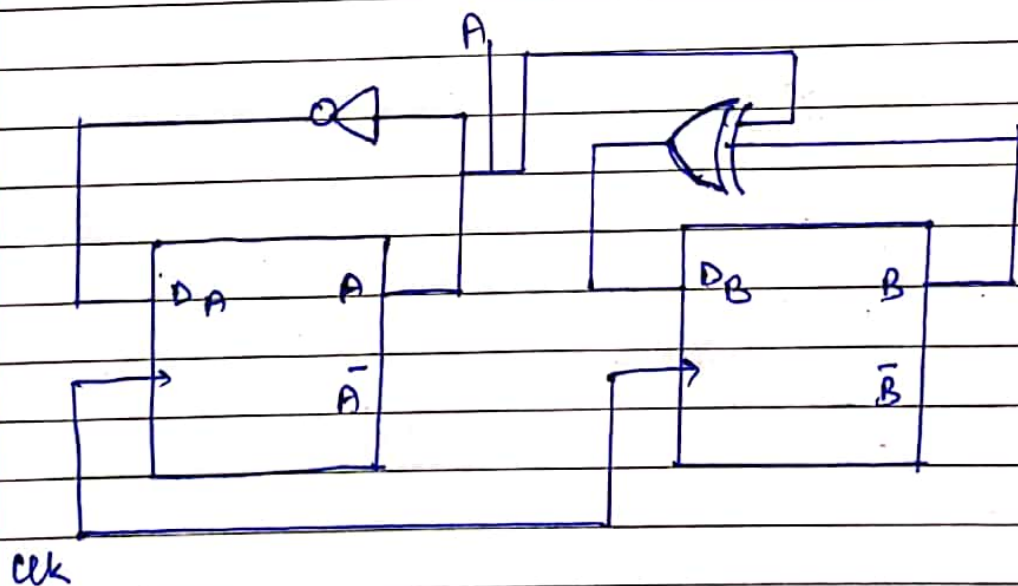


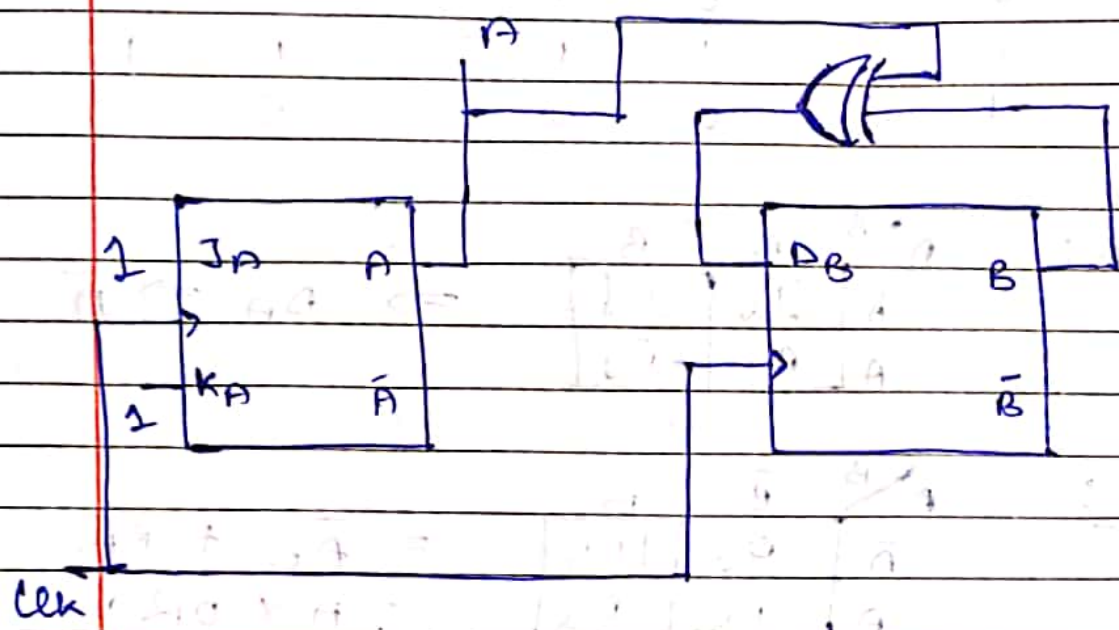iii) Using JK for MSB and DFF for LSB.

From above parts we know,  $J_A = 1$ ,  $K_A = 1$  &  
 $\Delta_B = A \oplus B$ .



Q3

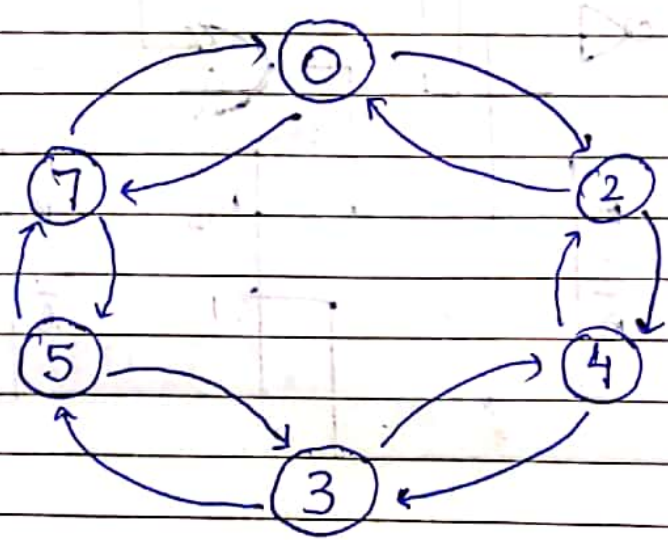

Present state			Imp	Next state			F.F		
A	B	C	Y	A	B	C	D <sub>A</sub>	D <sub>B</sub>	D <sub>C</sub>
0	0	0	0	1	1	1	1	1	1
1	1	1	0	1	0	1	1	0	1
1	0	1	0	0	1	1	0	1	1
0	1	1	0	1	0	0	1	0	0
1	0	0	0	0	1	0	0	1	0
0	1	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	1	0
0	1	0	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1	1
0	1	1	1	1	0	1	1	0	1
1	0	1	1	1	1	1	1	1	1
1	1	1	1	0	0	0	0	0	0

\*  $Y = 0 \rightarrow$  Down

$Y = 1 \rightarrow$  Up

For D<sub>A</sub>:

Y \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{Y}\bar{A}$	1	x	1	0
$\bar{Y}A$	0	0	1	x
$YA$	0	1	1	x
$Y\bar{A}$	0	x	1	1

$$D_A = BC + YC + YB + \bar{Y}\bar{A}\bar{B}$$



For  $\Delta_B$ :

$Y_A \backslash BC$	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{Y}_A$	1	X	0	0
$\bar{Y}_A$	1	1	0	X
$Y_A$	1	1	0	X
$Y_A$	1	X	0	0


$$\Delta_B = \bar{B}$$

For  $\Delta_C$ :

$Y_A \backslash BC$	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{Y}_A$	1	X	0	0
$\bar{Y}_A$	0	1	1	X
$Y_A$	1	1	0	X
$Y_A$	0	X	1	0

$$\Delta_C = Y_A \bar{A} C + Y_A \bar{A} \bar{B} + \bar{Y}_A A C + \bar{Y}_A \bar{A} \bar{B}$$

Q4

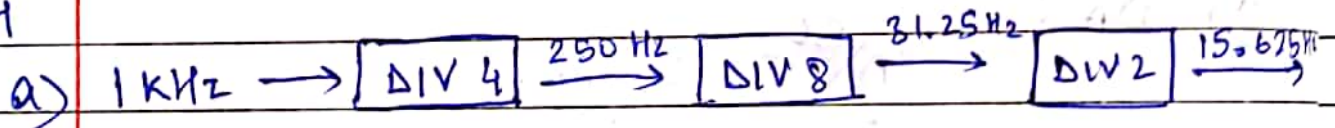


① = 250 Hz

② = 31.25 Hz

③ = 15.625 Hz

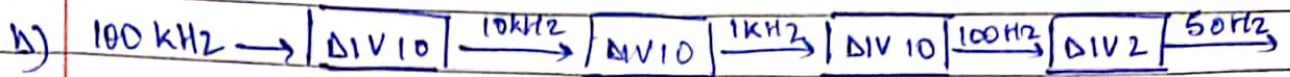⇒ Overall it is  $\text{MOD}(4 \times 8 \times 32) = \boxed{\text{MOD } 64 \text{ counter}}$



① = 10 kHz

② = 1 kHz

③ = 100 Hz

④ = 50 Hz

⇒ Overall it is MOD(10 × 10 × 10 × 2) = MOD 2000 counter

Q5 In the given circuit each flip flop get clock pulse at the same time. So when the clock is applied, in 50 ns all flip flop will give output + we need inputs for the next stage of flip-flops so additional 20 ns + 20 ns will be needed. So, minimum time period for clock = 50 + 20 + 20 = 90 ns

$$F_{\max} = \frac{1}{T_{\min}} = \frac{1}{90 \times 10^{-9}} = \frac{10^9}{90} = 0.0111 \times 10^9 \text{ Hz}$$

$$= \underline{\underline{11.1 \text{ MHz}}}$$